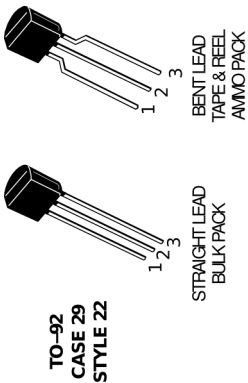



Instructions:

- 1) set V_IN to 1V (set current limit to 100mA)
- 2) connect sig gen to V_CONTROL, set for square wave, 5V amplitude, 10kHz frequency
- 3) Connect V_OUT to scope. Observe effect of adjusting duty cycle of V_CONTROL between 50% – 80%
- 4) observe effect of turning on and off V_CONTROL signal
- 5) remove R1 & D2, observe effect of turning on V_CONTROL (CAUTION!! HIGH VOLTAGE!!)
- 6) BONUS: Replace R1 & D2 with a single resistor, value >= 100.
- 7) BONUS: Using equation for duty cycle (below), do an experiment to work out efficiency (eta). Does eta depend on output voltage, input voltage or output load resistance? Any ideas why?

$$D = 1 - \eta \frac{V_{IN}}{V_{OUT}}$$



MARKING DIAGRAM AND PIN ASSIGNMENT

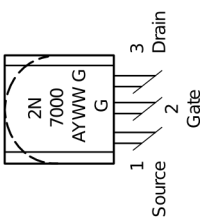

Dan Weatherill
Boost converter demonstrator

Sheet: /
File: converter.sch

Title: Oxhack analog electronics #3

Size: A4	Date: 2017-09-13	Rev: 0.1
KiCad E.D.A. eschema 4.0.7		Id: 1/1